

ECE571: Introduction to SystemVerilog

FALL-2025

Homework-1

By

Venkata Sriram Kamarajugadda

PSU ID: 901411425



`vkamaraj@pdx.edu`

*Department of Electrical & Computer Engineering
Maseeh College of Engineering & Computer Science
Portland State University*

Truth Table

Martian Calendar Days								
TRUTH TABLE								
Inputs					Outputs			
Month								
Encoded								
Month	M4	M3	M2	M1	M0	LY	D27	D28
Sagittarius	0	0	0	0	0	X	0	1
Dhanus	0	0	0	0	1	X	1	0
Capricornus	0	0	0	1	0	X	0	1
Makara	0	0	0	1	1	X	1	0
Awuarious	0	0	1	0	0	X	0	1
Kumbha	0	0	1	0	1	X	1	0
Pisces	0	0	1	1	0	X	0	1
Mina	0	0	1	1	1	X	1	0
Aries	0	1	0	0	0	X	0	1
Mesha	0	1	0	0	1	X	1	0
Taurus	0	1	0	1	0	X	0	1
Rishabha	0	1	0	1	1	X	1	0
Gemini	0	1	1	0	0	X	0	1
Mithuna	0	1	1	0	1	X	1	0
Cancer	0	1	1	1	0	X	0	1
Karka	0	1	1	1	1	X	1	0
Leo	1	0	0	0	0	X	0	1
Simha	1	0	0	0	1	X	1	0
Virgo	1	0	0	1	0	X	0	1
Kanya	1	0	0	1	1	X	1	0
Kibra	1	0	1	0	0	X	0	1
Tula	1	0	1	0	1	X	1	0
Scorpius	1	0	1	1	0	X	0	1
Vrishika	1	0	1	1	1	0	1	0
Vrishika	1	1	0	0	0	1	0	1
unused	1	1	0	0	0	X	X	X
unused	1	1	0	0	1	X	X	X
unused	1	1	0	1	0	X	X	X
unused	1	1	0	1	1	X	X	X
unused	1	1	1	0	0	X	X	X
unused	1	1	1	0	1	X	X	X
unused	1	1	1	1	0	X	X	X
unused	1	1	1	1	1	X	X	X

D27 K-Map

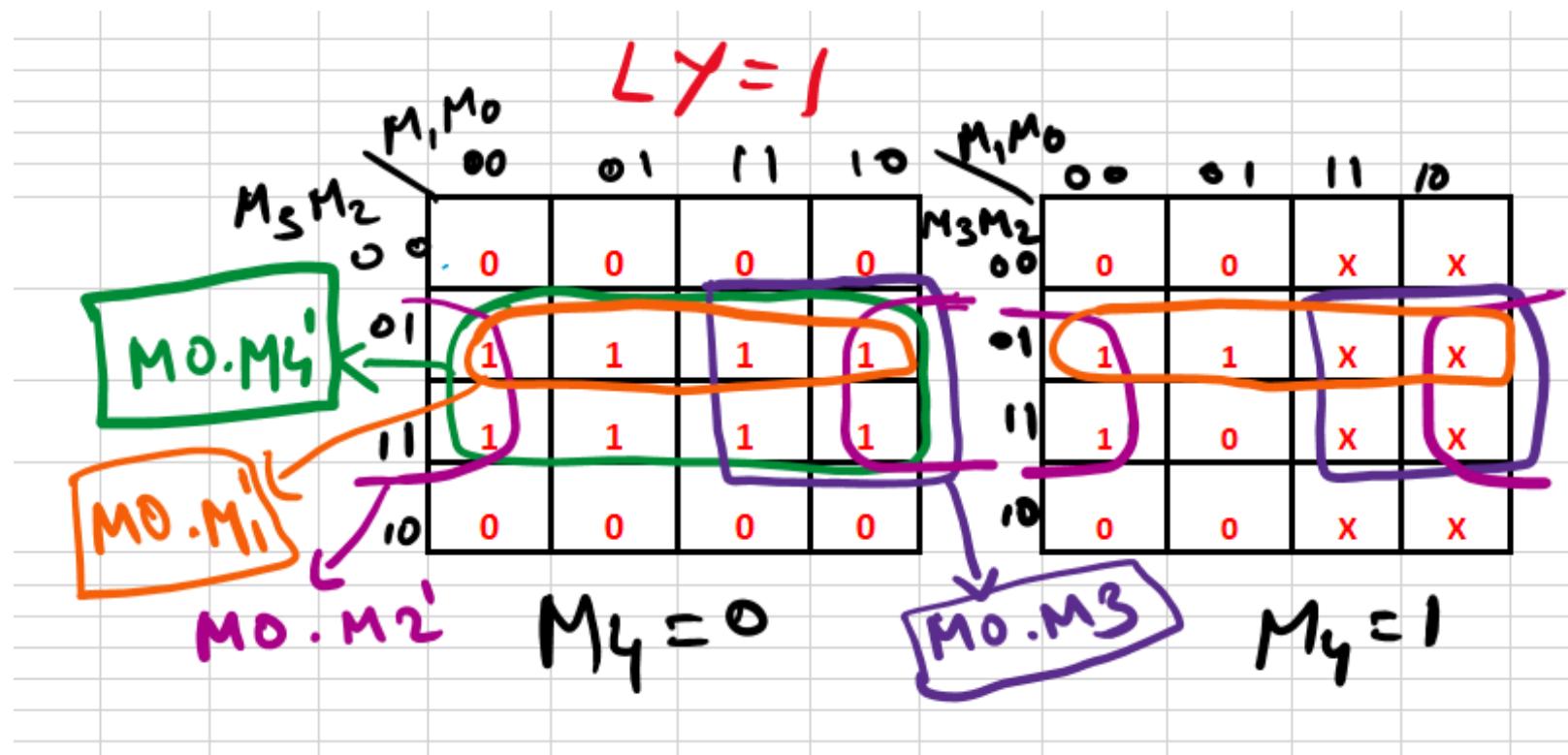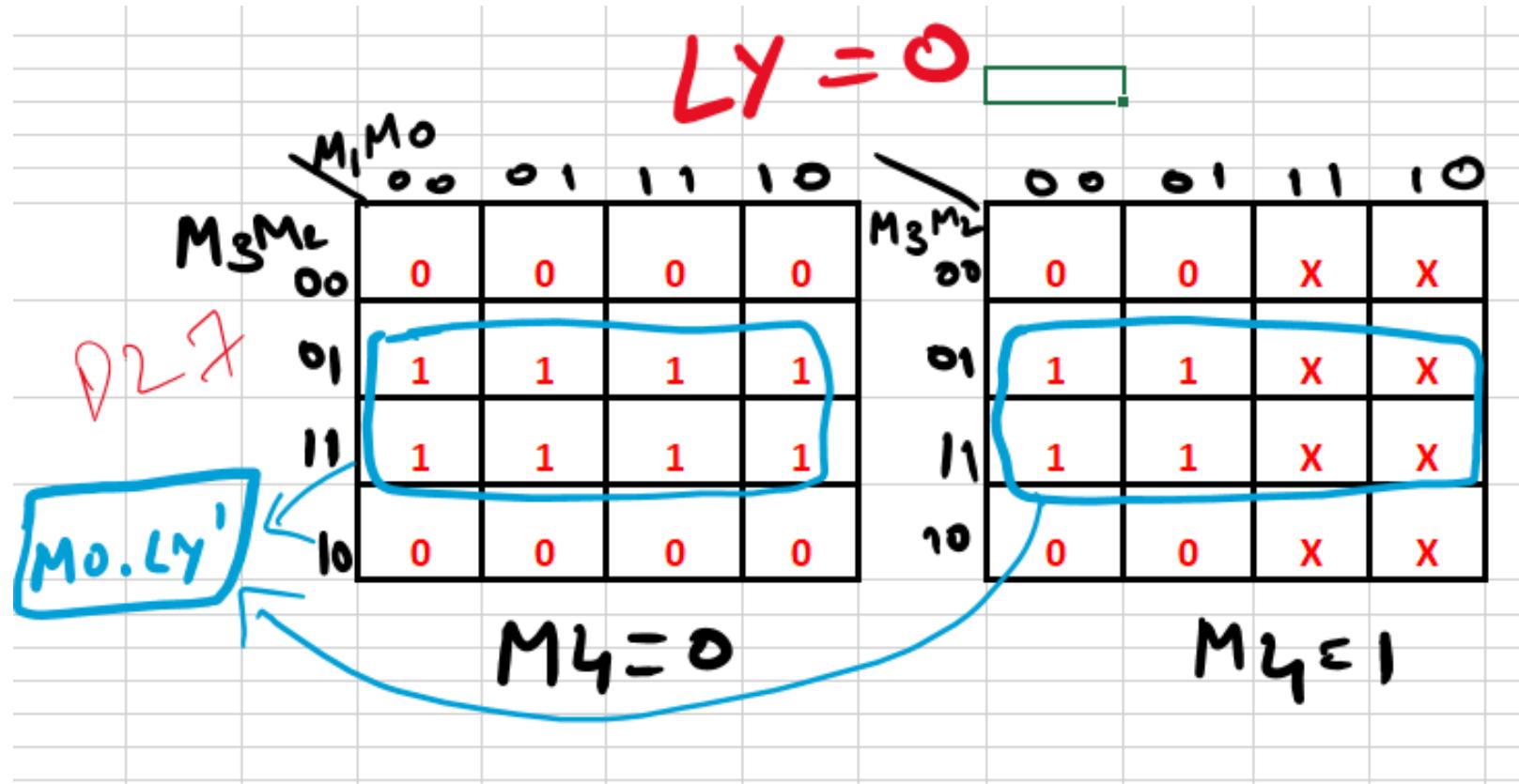



From above eq's $\Rightarrow D27 = M_0 \cdot LY' + M_0 \cdot M_4' + M_0 \cdot M_3 + M_0 \cdot M_2' + M_0 \cdot M_1'$

~~$D27 = M_0 (M_1' + M_2' + M_3 + M_4' + LY')$~~

$$D27 = M_0 \cdot LY' + M_0 \cdot M_4' + M_0 \cdot M_3 + M_0 \cdot M_2' + M_0 \cdot M_1'$$

$$D27 = M_0(LY' + M_4' + M_3 + M_2' + M_1)$$

D28 K-Map

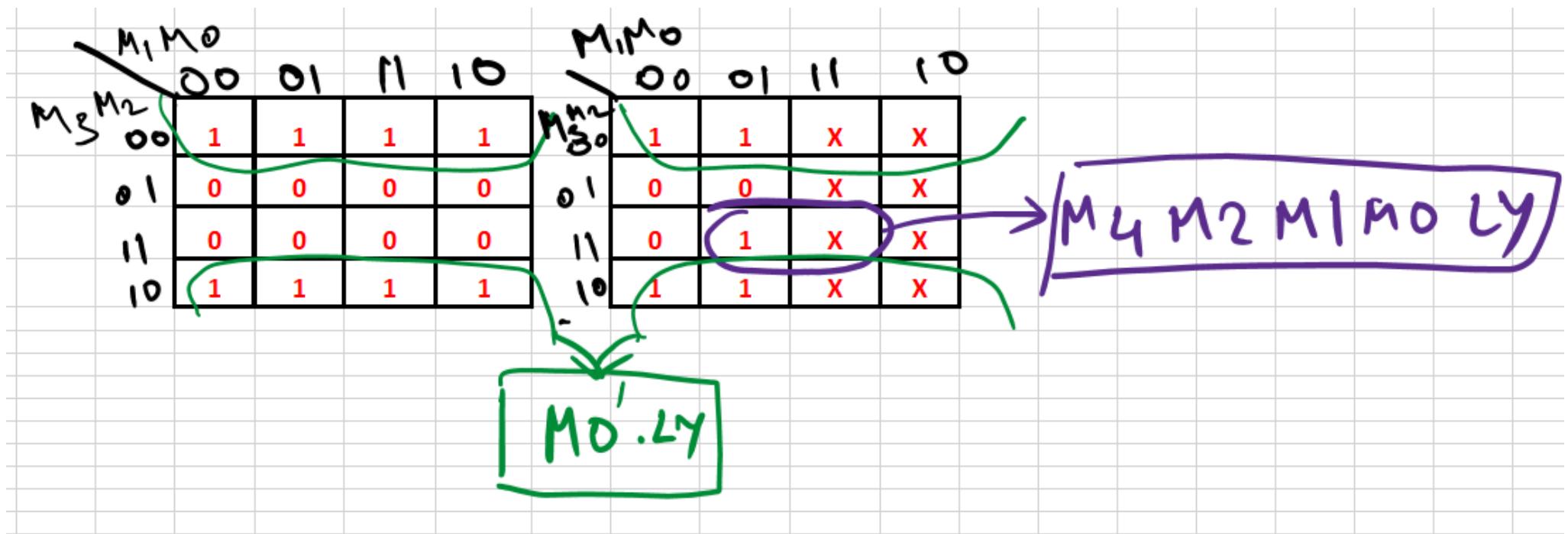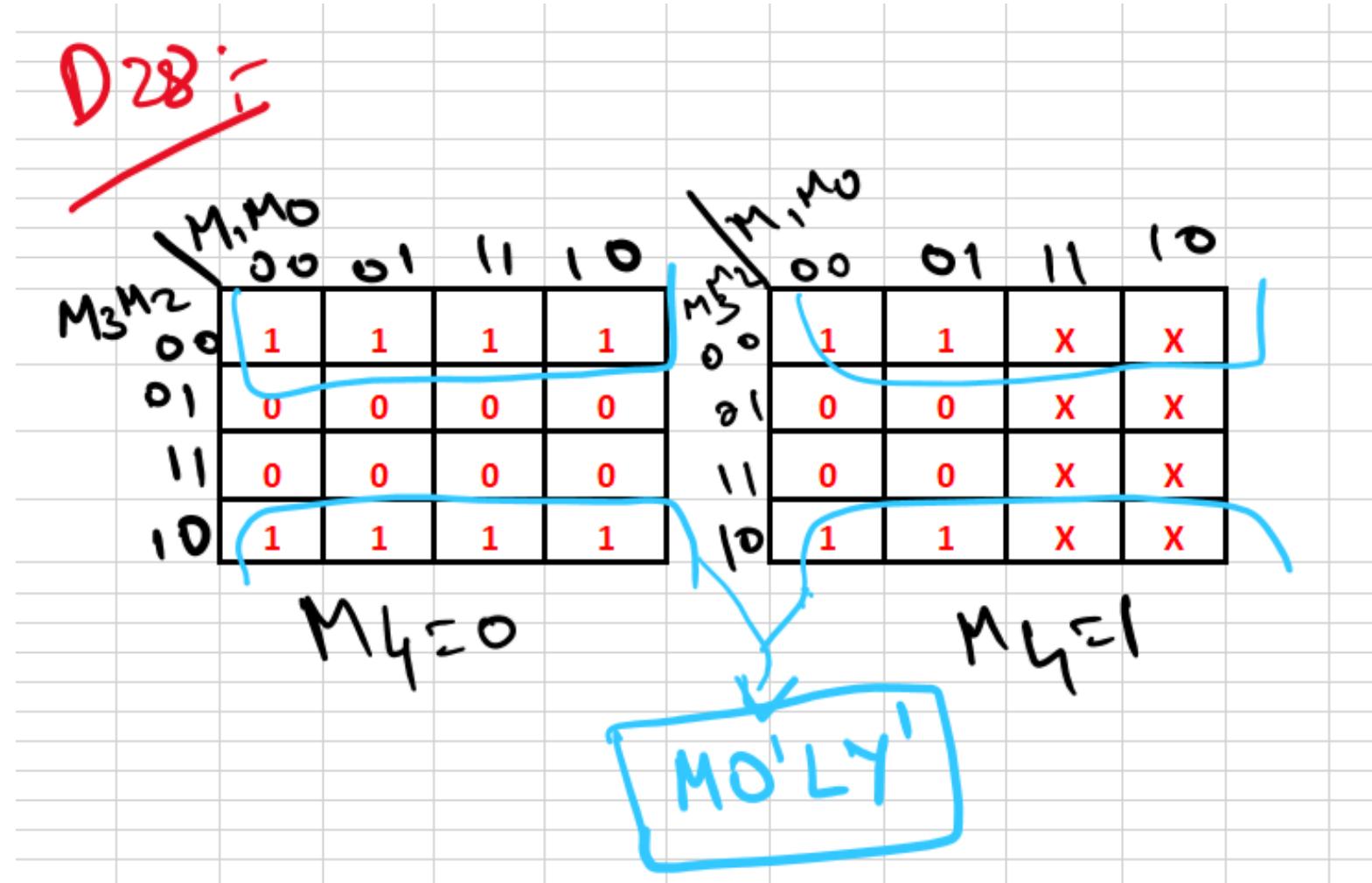


From above eq's:- $D28 = M_0' L Y' + M_0' L Y + M_4 M_2 M_1 M_0 L Y$
 $= M_0' (L Y' + L Y) + M_4 M_2 M_1 M_0 L Y$

$D28 = M_0' + M_4 M_2 M_1 M_0 L Y$

$D28 = M_0' L Y' + M_0' L Y + M_4 M_2 M_1 M_0 L Y$

$D28 = M_0' + (M_4 M_2 M_1 M_0 L Y)$

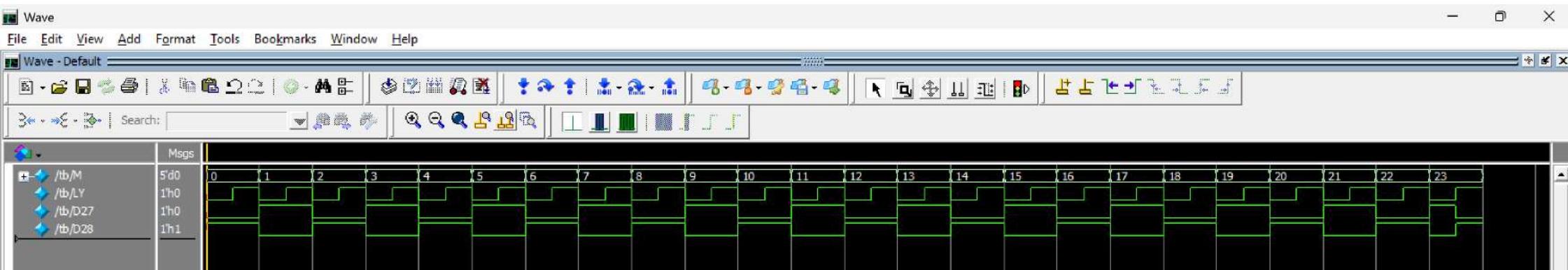

Thank You